

## 1 General introduction

Recall that after *Architectural Synthesis*, we had *Logic Synthesis*.

Logic synthesis consisted of the following sub-steps ...

1. Logic Optimization
  - 1.1. Minimizing undesirable redundancies; Using K-Maps, boolean identities, etc...
2. Technology Mapping (ie. Library Binding)
  - 2.1. Mapping logic to library cells
  - 2.2. The 'binding' that is going on here is of a **microscopic** level, in contrast to the **macroscopic** 'binding' that happened during architectural synthesis

We will focus on Technology Mapping now.

## 2 Introduction to Technology Mapping

Maps the technology **independent** network resulting from logic optimization, to logic cells that are available in a technology **dependent** cell library

Whilst performing technology mapping, we utilize algorithms to further minimize area while still meeting constraints (eg. timing constraints).

### 2.1 Types of technology mapping

Broadly speaking, it depends on whether we are developig for ASICs or FPGAs.

- ASICs
  - Usually library cells are more primitive than that of FPGAs
  - Limited set of pre-designed cells
- FPGAs
  - LUT-based (Xilinx): Each FPGA cell is termed a *Configurable Logic Block*
  - MUX-based (Actel): Each FPGA cell consists of a number of multiplexers

#### 2.1.1 (ASIC) cell library

As an example, the IBM standard-cell library used for the POWER4 is as follows

 


Figure 1: Designer has the following cells to build upon

## 2.1.2 (FPGA) LUT-based cells

### 2.1.2.1 Multiplexer

Let's begin with a 4-1 MUX.

 


Figure 2: 4-1 MUX, with associated truth table

- In a 4-1 MUX, we have 2 *selection* signals which select amongst  $2^2$  *input* signals.
- Note that **each** of the  $\{I_0, I_1, I_2, I_3\}$  signals could be 0 or 1, therefore this 4-1 MUX has  $2^{2^{num\_input\_signals}} = 16$  possible **input-output** combinations.
- Recognize that a *logic function* is a *mapping* from input to output (singular in this case), hence we could represent 16 different combinational functions this way.
- Herein is the underlying logic behind an LUT - if we can configure the value of these input signals, then we can construct 16 different combinational functions.

### 2.1.2.2 Constructing an LUT

Using the ideas above, the 4-1 MUX above can thus be converted into a 2LUT (2-input LUT)

 


Figure 3: 2LUT

*Selection signals are our input addresses*

 


Figure 4: **0110** represents the **output** of a particular truth table (ie. combinational function) that this 2LUT implements

- The LUT consists of a block of SRAM that is indexed by the LUT's inputs
- Output of the LUT is whatever value is in the indexed location in it's SRAM

Let's examine the internals of the LUT.

- LUT is built out of ...
  1. SRAM bits to hold some configurable memory (*CRAM*), we term this the *LUT-mask*
  2. Set of multiplexers to select the bit of CRAM that will be directed to output
- To implement a k-LUT (an LUT that can implement any k-input function), we require ...
  1.  $2^k$  SRAM bits. Note that there are  $2^{2^k}$  possible combinational functions, but we are setting the SRAM bits (ie. outputs) only for a **certain** combinational function we want to implement. Therefore, since the combinational function has  $k$  inputs, it should have  $2^k$  possible outputs.
  2.  $2^k : 1$  MUX, to select the output for our **certain** combinational function

 


Figure 5: 4LUT

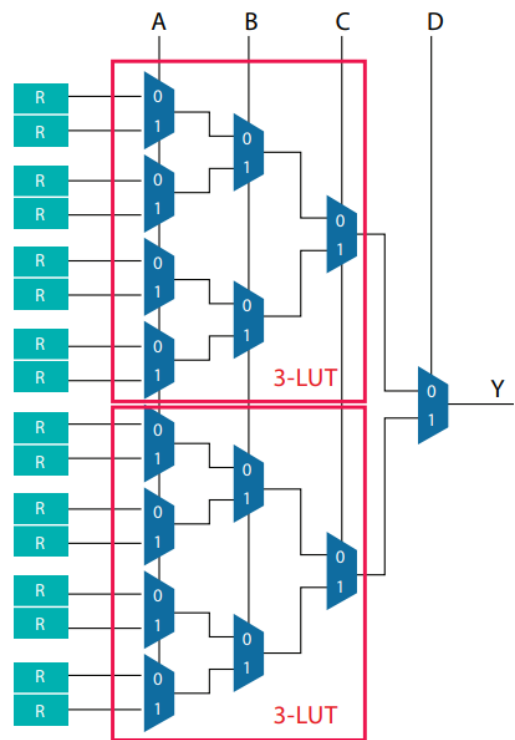


Figure 6: 4LUT implemented with two 3LUT and a 2:1 MUX

### 2.1.2.3 CLB

Finally, we can understand how the CLB is built.

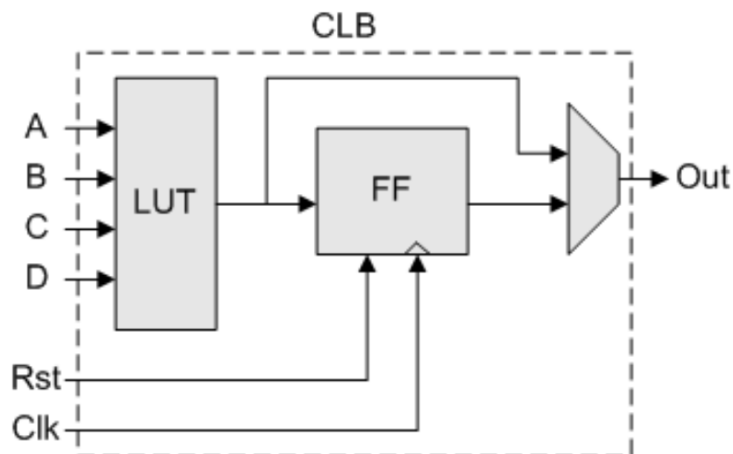


Figure 7: Configurable Logic Block

### 2.1.3 (FPGA) MUX-based cells

#### 2.1.3.1 Tweaking the Multiplexer

Remember the 4-1 MUX earlier?

 


Figure 8: 4-1 MUX

Previously, the 4-1 MUX could only implement a 2-input combinational function (via  $\{S_0, S_1\}$ ), since  $\{I_0, I_1, I_2, I_3\}$  were 'fixed' at binary values 0 or 1. However, what if we allowed  $\{I_0, I_1, I_2, I_3\}$  to act as inputs as well? Then the 4-1 MUX can implement up to a 6-input combinational function!

Hence, we can further expand on the truth table of the MUX.

 


Figure 9: 2-1 MUX

Configuration			F=
A	B	S	
0	0	0	0
0	X	1	X
0	Y	1	Y
0	Y	X	$X\bar{Y}$
X	0	Y	$X\bar{Y}$
Y	0	X	$\bar{X}Y$
Y	1	X	$X + Y$
1	0	X	$\bar{X}$
1	0	Y	$\bar{Y}$
1	1	1	1

Figure 10: Expanded truth table.

Note that it is non-exhaustive, since we expect there to be  $3^3$  possible combinations

This new way of viewing MUXes will make sense soon.

### 2.1.3.2 Shannon's decomposition theorem

Allows for any logic function to be expanded and broken down into parts. This means that it is possible to implement any logical function using multiplexers.

$$\begin{aligned}
 f(x_1, x_2, \dots, x_n) &= x_1 \cdot f(1, x_2, \dots, x_n) + \bar{x}_1 \cdot f(0, x_2, \dots, x_n) \\
 &= (x_1 + f(0, x_2, \dots, x_n)) \cdot (\bar{x}_1 + f(1, x_2, \dots, x_n)) \\
 &= x_1 \cdot f(1, x_2, \dots, x_n) \oplus \bar{x}_1 \cdot f(0, x_2, \dots, x_n)
 \end{aligned}$$

Figure 11: Shannon's decomposition theorem

Let's apply Shannon's decomposition theorem now.

1. Suppose we have a function  $F(a, b, c)$
2. Expanding it using SDT, we get  $F = a \cdot F_a + \bar{a} \cdot F_{\bar{a}}$
3. Therefore,  $F$  can be implemented as a 2-1 MUX as seen below.

 


Figure 12: When  $a = 1$ ,  $F_a$  is channeled to output  
When  $a = 0$ ,  $F_{\bar{a}}$  is channeled to output

We can recursively apply SDT ...

1.  $F = a \cdot F_a + \bar{a} \cdot F_{\bar{a}}$

- 1.1.  $F_a = b \cdot F_{ab} + \bar{b} \cdot F_{a\bar{b}}$
- 1.2.  $F_{\bar{a}} = b \cdot F_{\bar{a}b} + \bar{b} \cdot F_{\bar{a}\bar{b}}$
2.  $F = \{a \cdot (b \cdot F_{ab} + \bar{b} \cdot F_{a\bar{b}})\} + \{\bar{a} \cdot (b \cdot F_{\bar{a}b} + \bar{b} \cdot F_{\bar{a}\bar{b}})\}$
3.  $F = \{a \cdot b \cdot F_{ab} + a \cdot \bar{b} \cdot F_{a\bar{b}}\} + \{\bar{a} \cdot b \cdot F_{\bar{a}b} + \bar{a} \cdot \bar{b} \cdot F_{\bar{a}\bar{b}}\}$

 


Figure 13: We see a 'tree' of MUXes forming...

#### 2.1.3.3 Logic modules

Actel uses the above MUXes to form MUX-based logic cells.

 


Figure 14: Implementation of combinational logic, using what Actel terms *ACT1 Logic Module*

## 2.2 Flow of Technology Mapping

Technology Mapping can be broadly broken down into 3 steps ...

### 1. Decomposition

- Restructures the logic network **and library cells** using **base** primitives
- The purpose of this is so that *pattern matching* at the later stage will be easier (since they are all expressed in terms of the same base primitives)
- Decomposition to base primitives decreases the level of optimization that can be done (tradeoff for increased simplicity)

### 2. Partitioning

- Partitions the large network into smaller sub-networks
- The purpose of this is so that the *Matching and Covering* stage is easier to handle (ie. divide and conquer strategy)
- Partitioning introduces module boundaries, decreasing the level of optimization that can be done (tradeoff for increased simplicity)

### 3. Matching and Covering

- Determines which library cells may be used to implement a set of nodes in our logic network

## 3 Logic Decomposition

We decompose the logic network **and library cells** using a choice of base primitives, which creates a new representation.

Note that logic decomposition is a heuristic that does not provide unique solutions.

 


Figure 15: *NAND2* and *INV* gates are popular choices for base primitives, since **every** boolean function can be implemented with a **combination** of them

Figure 16: Decomposed library cells (of the IBM POWER4). We term these *Pattern Trees*

Suppose we have a complex gate in our logic network, shown below.

 


Figure 17: *NAND4* gate may be decomposed in two different ways

We note that the two decompositions are *functionally* identical, but *structurally* (and hence timing-wise) different. Therefore, complex gates may be *matched* by completely different patterns.

## 4 Partitioning

- Reduce a *MIMO* (multi-input-multi-output) network into a collection of *MISO* (multi-input-single-output) sub-networks, with each sub-network termed as a *subject graph*
- This allows for a *Divide and Conquer* approach to the *Covering problem* that we will see later

### 4.1 Partitioning algorithm

1. Mark vertices with multiple-out degrees; Edges connected to these marked vertices define the partition boundary
2. Partition accordingly to form *subject graphs* (ie. break the circuit at fanout points)
3. Note that we may further (recursively) partition the subject graphs

 


Figure 18: Partitioned graph

## 5 Pattern Matching and Covering

There are two main types of pattern matching ...

- Structural Matching
- Boolean Matching

### 5.1 Structural Matching

Intuitively, it is matching by looking at shapes. We match the logic network with the library cells recursively, until the entire network is mapped.

 


Figure 19: Possible matches (depending on which library cell we map to)

 


Figure 20: Library cells available

As seen in the example above, there may be multiple matches available for the same set of nodes. We need an algorithm to find which are the best matches that we eventually use to cover the entire network.

### 5.1.1 Recursive algorithm for Structural Matching

Recursive algorithm to identify if *pattern tree* (decomposed library cells) is *isomorphic* (ie. same shape) to a subgraph of the subject tree. Note that it works only when **one** type of base primitive is used in the decomposition (further note: *Inverter* can be seen as *NAND* gate with inputs shorted).

#### 5.1.1.1 Some definitions before we get started

Note that orientation of the tree!

- Degree of vertex used to indicate the number of children
- $u$  is the root of the **pattern** graph
- $v$  is a vertex of the **subject** graph

 


Figure 21: Vertex with degree=2

#### 5.1.1.2 Algorithm

```

Match (u,v){
    if (u is a leaf) return (true);           //Matches isomorphic graphs too
    else {                                    //Leaf of pattern graph
        if (v is a leaf) return (false);      //Leaf of subject graph
        if (degree(v)≠degree(u) return (False); //Different gate
        if (degree(v)==1){
            uc = child of u; vc = child of v;
            return (Match(uc, vc));          //Recursive call
        }
        else{
            ul = left-child of u; ur = right-child of u;
            vl = left-child of v; vr = right-child of v;
            return (Match(ul, vl).Match(ur, vr) + Match(ur, vl).Match(ul, vr));
        }
    }
}

```

Figure 22: Recursive algorithm for matching

#### 5.1.1.3 Algorithm - Example 1

 


Figure 23: Subject graph, with corresponding circuit



 


Figure 24: Pattern graph, with corresponding circuit

 

 

- If we start from vertex  $v_1$  of the subject graph, then we have that  $degree(v_1) = 1 \neq degree(u) = 2$ . Therefore no match.
- If we start from vertex  $v_2$  of the subject graph (assume that  $v_1$  was matched by other library cells), then we have that  $degree(v_2) = 2 = degree(u) = 2$ . Therefore match *might* be possible. We will enter the *else* statement for further checks, eventually finding that match is possible.

#### 5.1.1.4 Algorithm - Example 2

We need to find all possible patterns in the subject network first, before we can decide which combination of patterns is optimal.

 


Figure 25: Subject network

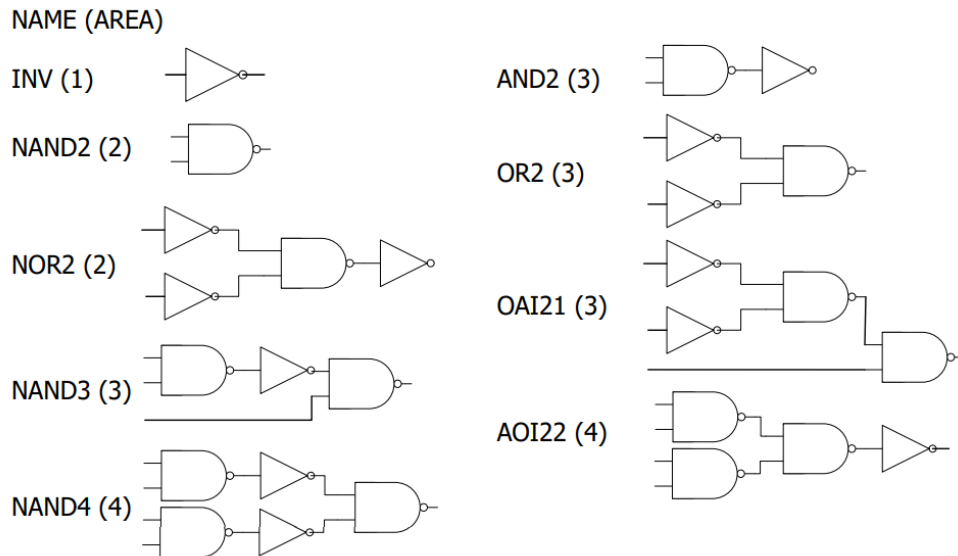


Figure 26: Cell Library

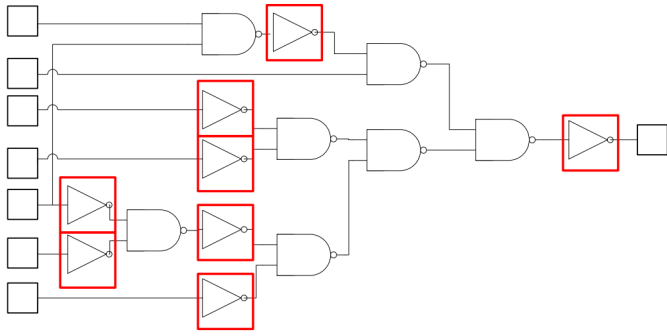


Figure 27: *INV* patterns

 


Figure 28: *NAND2* patterns

 


Figure 29: *AND2* patterns

 


Figure 30: *OR2* patterns

 


Figure 31: *NOR2* patterns

 


Figure 32: *NAND3* patterns

 


Figure 33: *OAI21* patterns

 


Figure 34: *AOI22* patterns

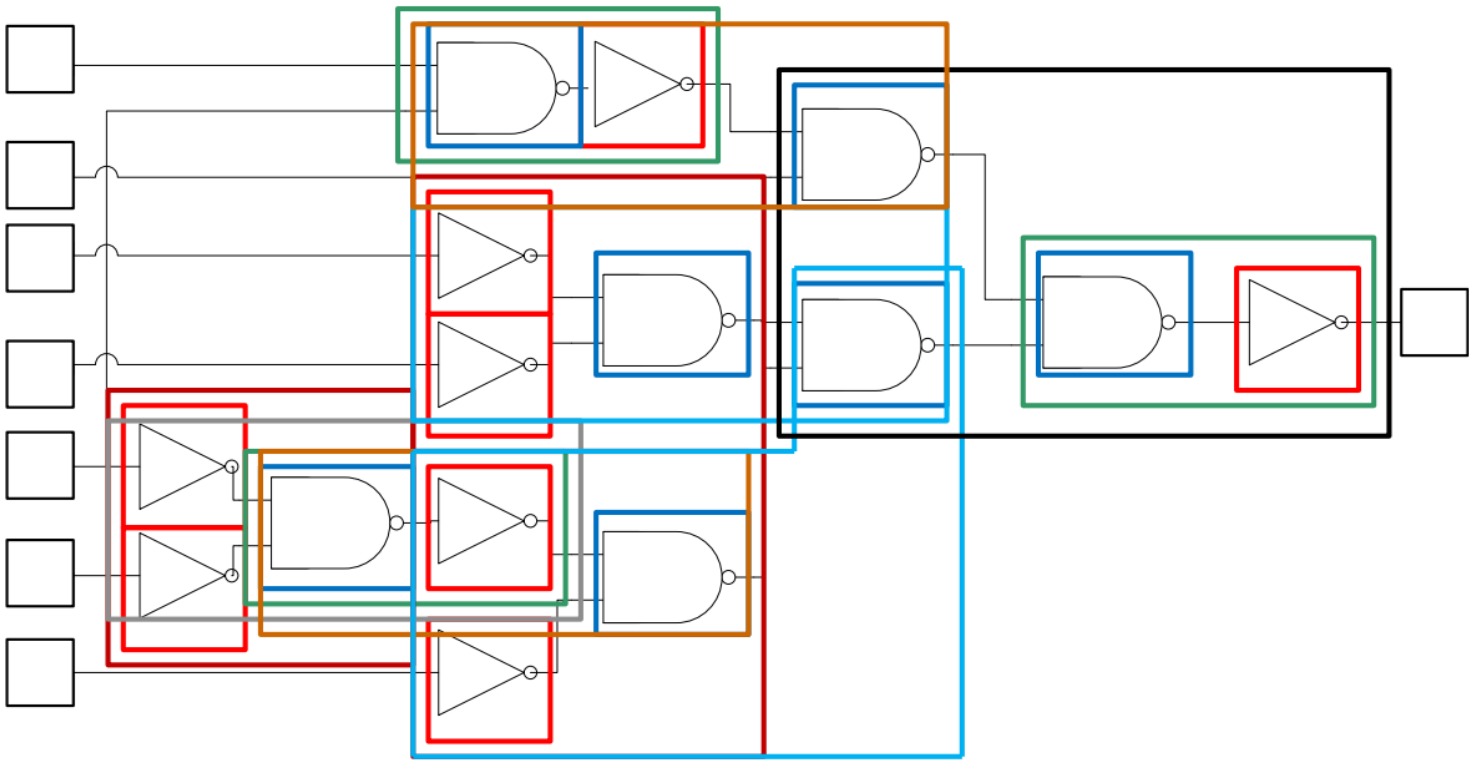


Figure 35: All patterns (superimposed)

Now the question of *optimal coverage*. Which different combinations shall we use to map the entire network?

- Note that a *greedy* approach **may not be optimal**.
- We have to try out all different combinations and see which is optimal. This will be covered later.

## 5.2 Problems with Structural Matching

### 5.2.1 Structural Matching works on trees only

#### 5.2.1.1 Recap: Properties of trees

- Each node in the tree can be connected to many children, but must be connected to **exactly one parent** (except for the root node).
- This constraint means that there are no 'cycles' or 'loops' in the tree
- What implications does this have for us?
  - Circuits with a **fan-out** node cannot be represented with a tree
  - Therefore, we cannot apply *matching* across fan-out nodes!

 


Figure 36: Not a tree. Node 4 has more than one parent.

 


Figure 37: Circuits with fan-out nodes are an issue

This means that *XOR* gates cannot be matched, since *XOR* gates require fan-out (by definition)

 


Figure 38:  $A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$ ; Thus *XOR* gates require fan-out

### 5.2.2 Structural Matching has imperfect matching

- Different structures **with the same functionality** are not identified by structural matching.
- This means that we miss out on potential matches, meaning our final result is not fully optimized

 


Figure 39:  $g = xy + \bar{x}y + xz$

 


Figure 40:  $f = xy + \bar{x}y + yz$

In the example above, both functions  $f$  and  $g$  are **functionally identical** (you can check using truth table), but **structurally different**. Structural matching will not identify that they are the same.

The fix to this issue is to do matching by *boolean logic*, rather than by *structure* (ie. isomorphism). This is called *Boolean Matching*.

## 6 Boolean Matching

Boolean Matching relies on matching the *pattern* to the *subject* logically

- Decomposition independent
- Patterns match via *structural match*  $\implies$  Patterns match via *boolean match*
  - Structurally matched pattern must be logically equivalent
- Patterns match via *boolean match*  $\not\implies$  Patterns match via *structural match*
  - Two logically equivalent patterns may have different structures (as we saw in Fig39 and Fig40)

### 6.1 Boolean Matching - General ideas

1. Define the *cluster function* (what we previously termed *subject graph*) as  $f(X) = f(x_1, x_2, \dots, x_n)$ ; ie.  $n$  input variables
2. Define the *pattern function* (what we previously termed *pattern graph*) as  $g(Y) = f(y_1, y_2, \dots, y_m)$ ; ie.  $m$  cell inputs
3. WLOG, assume  $n = m$
4. Matching of functions  $f$  and  $g$ , involves comparing  $f$  and  $g$  for *equivalence* (ie. checking if they are logically equivalent)
  - 4.1. Intuitively, we are examining all *permutations* to find valid assignment(s) of variables from **cluster function** to variables of **pattern function**

 


Figure 41: Abstracted view of cluster and pattern functions

 


Figure 42: There are many different ways (*permutations*) to connect  $\{x_1, \dots, x_n\}$  with  $\{y_1, \dots, y_n\}$ . We need to examine all permutations to find if logical equivalence exists (and if so, under which case is it mapping is it optimal?)

 


Figure 43: One possible connection might be this. Note that  $y_1$  of pattern function does not correspond to  $x_1$  of cluster function

## 6.2 Equivalence of functions

Functions may be logically equivalent under different conditions, let's examine an example.

### 6.2.1 Permutation of input variables

Ordering of input *cluster variables* needs to be changed

 
 


Figure 45: One possible permutation that is valid

Figure 44: Can desired functionality be implemented with library cell?

Mathematically speaking, we have  $g(Y) = f(\rho(X))$  where  $\rho$  is some permutation of  $X$

For example ...

1. Suppose  $f(X) = x_1\bar{x}_3 + x_2x_4$
2. Suppose  $g(Y) = y_2\bar{y}_4 + y_1y_3$
3.  $\rho$  reorders  $X$  and maps ...
  - 3.1.  $x_1 \rightarrow y_2$
  - 3.2.  $x_2 \rightarrow y_1$
  - 3.3.  $x_3 \rightarrow y_4$
  - 3.4.  $x_4 \rightarrow y_3$
4. Hence,  $g(Y) = f(\rho(X))$

If functions are equivalent when variable order is allowed to change, we term that *P-equivalent*

### 6.2.2 Negation of input variables

Polarity of inputs can be altered, assuming that inputs come from FFs (which provide input and its complemented version)

 
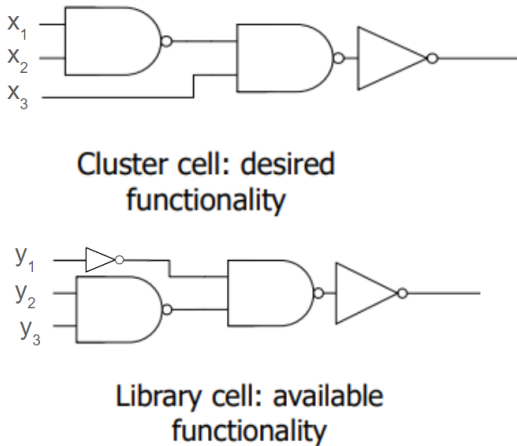


Figure 47: However, taking  $\bar{Q}$  from the input FF solves our problems

Figure 46: We cannot directly connect cluster variables to pattern variables now

Mathematically speaking, we have  $g(Y) = f(\phi(X))$  where  $\phi$  maps  $x_i$  (elements of  $X$ ) either to  $y_i$  or  $\bar{y}_i$

For example ...

1. Suppose  $f(X) = x_1 + x_2 + x_3$
2. Suppose  $g(Y) = \bar{y}_1 + \bar{y}_2 + y_3$
3.  $\phi$  maps ...
  - 3.1.  $x_1 \rightarrow \bar{y}_1$
  - 3.2.  $x_2 \rightarrow \bar{y}_2$
  - 3.3.  $x_3 \rightarrow y_3$
4. Hence,  $g(Y) = f(\phi(X))$

If functions are equivalent when polarity of input variable is allowed to change, we term that *N-equivalent*

### 6.2.3 Negation of output variables

Same concept of negation of input variables, but this time at the output

For example ...

1. Suppose  $f(X) = x_1 + x_2$
2. Suppose  $g(Y) = \bar{y}_1 \cdot \bar{y}_2$
3. Do  $g(Y) = \bar{f}(X)$

### 6.2.4 Summary

We thus have three categories of equivalence ...

- *NPN-equivalent*: Equivalent under input negation, input permutation, output negation
- *PN-equivalent*: Equivalent under input permutation, output negation
- *P-equivalent*: Equivalent under input permutation

In the **worst-case** scenario of *NPN-equivalence*, we have to check  $(2^n \times n! \times 2)$  mappings just to determine if logical equivalence exists!

- $2^n$ :  $n$  input variables may be negated (either 0 or 1)
- $n!$ :  $n$  input variables have  $n!$  different permutations (orderings)
- 2: output variable may be negated (either 0 or 1)

That is alot of mappings to consider. *Boolean signatures* give us a way to reduce the number of possibilities.

## 7 Boolean Signatures

Boolean signatures are a compact representation that characterizes **some** of the properties of a boolean function.

- Boolean signatures do not match  $\implies$  No match is possible
- Boolean signatures match  $\implies$  Match **may** be possible
  - Each boolean function has a **unique** signature, but a signature can be related to  $> 1$  functions (this problem is termed *aliasing*)
  - Therefore, signature matching is *necessary*, but **not** a *sufficient* condition
  - Only if **all** possible boolean signatures match, then we can say that function match is possible (but this is not a practical way to do so)

Therefore, the main idea is to use some simple boolean signatures to filter out the solution space, before we start checking function equivalence. If we know that some functions already have non-matching boolean signatures, we need not consider them during the function equivalence stage.

Note that whether the boolean signatures match, also depends on equivalence type we are checking for (NPN, PN, P)?

## 7.1 Example of boolean signatures

### 7.1.1 Function symmetry

How many sets of variables are pairwise interchangeable without affecting the logic?

- $\bar{A}\bar{B} + ABC$ ;  $A, B$  are pairwise interchangeable (1 set)
- $\bar{B}(A + \bar{C}) + C$ ; No variables are pairwise interchangeable (0 set)

### 7.1.2 Number of unate/binate variables

- Unate variables: Variables with which a function *monotonically* increases/decreases
- Binate variables: Not unate variables

An example ...  $A\bar{C} + \bar{A}B$

- $B, C$  are unate variables ( $B$  **always** pulls towards logic high,  $C$  **always** pulls towards logic low)
- $A$  is binate variable ( $A$  can pull to logic high or low, depending on circumstances)

## 7.2 Summary

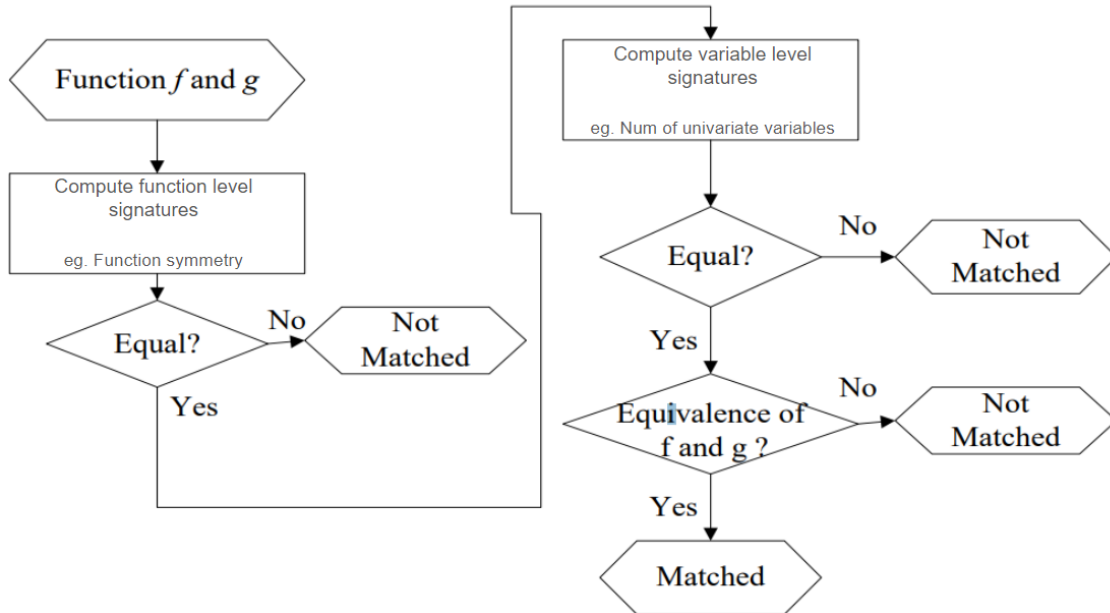


Figure 48: Flowchart

## 8 Covering

Once we find matches between the pattern-tree (decomposed library cells) and subgraphs of the subject tree, which match shall we pick to implement our actual circuit?

Formally speaking ...

- Define *covering* as a collection of pattern graphs st. every node of the subject graph is contained in one (or more) of the pattern graphs
- We then want to find the **minimum** cost covering - which particular collection of pattern graphs will achieve this?



## 8.1 Covering of trees and DAGs

### 8.1.1 Trees

 


Figure 49: Cell Library

 


Figure 50: Subject graph **with no fanout nodes**

- Consider the example above, where the subject graph **has no fanout nodes**.
- We know that we can convert the subject graph to a *tree*, since there are no fan-out nodes
- We also know that we can convert the cell library to its appropriate tree representation
- Therefore, the covering problem to cover the 'subject-tree' using 'pattern-trees', which **has a P solution**.

 


Figure 51: Trivial covering

 


Figure 52: Better covering

 


Figure 53: Even better covering

### 8.1.2 DAGs

 


Figure 54: *XOR* gate

 


Figure 55: *XOR* gate representation - DAG

Covering a 'subject-DAG' using a 'pattern-tree' is termed *DAG-covering*, and is **NP-hard**.

#### 8.1.2.1 Treeifying

Partitioning a circuit with fan-out nodes (ie. DAG) at the fan-out node points, thereby forming a collection of **trees**.

 


Figure 56: DAG is now transformed into a collection of subnetworks, where each subnetwork is a tree

- We can then use  $P$  solution of tree-covering on each of these sub-networks.
- The tradeoff is lowered optimization - We are not able to do inter-subnetwork optimizations

Also note that when the DAG is broken into trees at the fan-out points, some of the logic is duplicated.

 


Figure 57: DAG  
( $\exists$  route between leaf(input) to **two** roots(outputs))

 


Figure 58: Logic at fan-out node is duplicated

## 8.2 Optimal tree covering using Dynamic Programming

- We use the *memoization* DP approach, visiting the subject tree **bottom-up** (it's easier this way)
- At each vertex, we attempt to match the **locally** rooted sub-tree to all library cells
  - Find the best match and record it at the vertex (ie. Memoization)
- Work your way up to the root

### 8.2.1 DP example

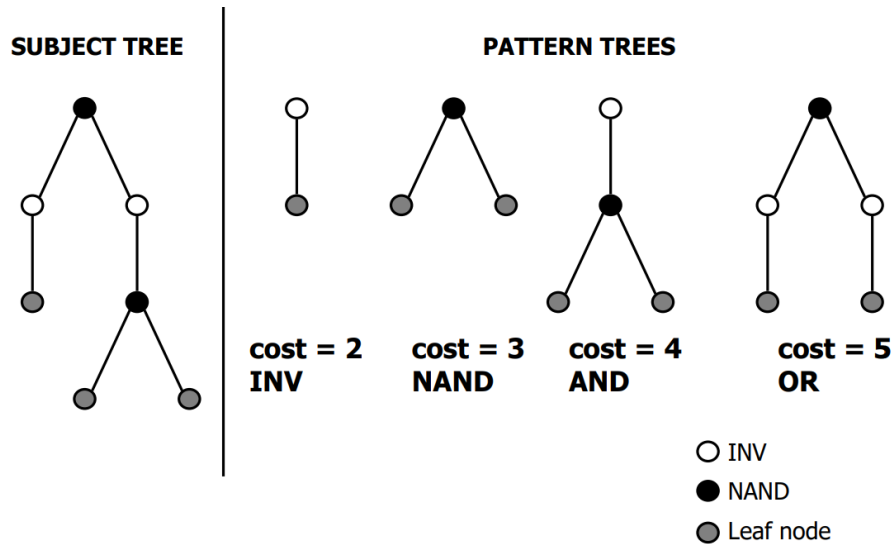


Figure 59: Subject and Pattern trees

 


Figure 60: Optimally cover the Subject tree using Pattern trees  
Approach this using DP (Memoization)

## 9 Technology Mapping on FPGAs

For FPGAs, the library cells are *LUTs* (higher abstraction level than ASICs).

### 9.1 How to do matching with LUTs?


Unlike previous sections, we do not decompose CLBs (library cell of FPGAs) using primitives (eg. *NAND2* and *INV*) and try to match using them, as it is not practical. For example, a 4-input LUT can implement  $2^{2^4} = 256$  possible combinational functions. Decomposing all 256 of those combinational functions is not a good idea.

So how do we match with LUTs? We simply configure the *LUT-mask* to match the output of the cluster function.

#### 9.1.1 LUT Matching - Example

Suppose we want to match a *NAND*-gate with a *4LUT*.

**NAND**



A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0

Figure 61: *NAND* truth table

We derive the truth table for a *4LUT* that matches the *NAND*'s truth table, and simply 'copy' *y* over to the *LUT-mask*.

x <sub>1</sub>	x <sub>2</sub>	x <sub>3</sub>	x <sub>4</sub>	y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Figure 62: Notice that  $x_3$  and  $x_4$  inputs are 'useless'

 


Figure 63: LUT-mask of 4LUT

We can see that it is very inefficient (in terms of hardware resources) to match the *NAND*-gate with a *4LUT*.

## 9.2 Mapping and Covering on FPGAs

Simply put, FPGA mapping involves transforming the original *subject* network into another network, where **every** node corresponds to an  $nLUT$  (where  $nLUT$  is the one afforded by our library cell).

Covering is then finding the optimal mapping to utilize, subject to some constraints (ie. use the minimal number of LUTs possible).

Assume that we have decomposed our subject network using whatever primitives were available. Below is how we would do FPGA mapping and covering ...

 


Figure 64: We require 3  $5LUT$ s or 6  $3LUT$ s to map & cover this circuit  
Notice that a  $5LUT$  can implement a  $4LUT$ , one of the inputs will just be 'X'

## 9.3 Bin Packing

- So far, all our SOP expressions can each 'fit' into a single LUT, but this is not always the case.
- Consider an SOP expression of a single-output function, suppose it has at most  $n$  variables
  - If we have an  $nLUT$ , then the **entire** SOP expression can be implemented by one  $nLUT$  (which is what we previously assumed)
- Suppose this SOP expression has  $> n$  variables now
  - If we only have an  $nLUT$ , then the SOP expression needs to be 'split' up and assigned to different  $nLUT$ s
  - This idea is similar (but not quite identical) to the *bin packing problem*, where we must pack a given set of objects (here product terms) of bounded size into bins (here tables)
- It is not exactly similar to the *bin packing problem*, since partitioning alone is not sufficient. We require **more bins** to hold the combined partitioned terms
  - Suppose *table size* is  $n = 3$  (ie. It's a  $3LUT$ )
  - Suppose *SOP expression* is  $f = ab + cd$
  - 2  $3LUT$ s are needed to implement  $ab$  and  $cd$ , but 1 more  $3LUT$  is needed to combine them together
  - Notice that there is room for optimization. For each  $3LUT$ , one of the inputs is unused. Could we squeeze additional logic into there? This leads us to *Modified Bin Packing*.

### 9.3.1 Modified Bin Packing (Heuristic algorithm)

- Iterate the following steps until all product terms have been 'binned'
  1. Select product term with the most variables

2. Place it into any table where it fits
3. If no table has enough place to fit it, create a new table and place it there
- When all product terms are 'binned', do the following steps
  1. Find the table  $t_i$  with the fewest number of **unused** variables (alternatively, table with most number of **used** variables) and associate a variable  $v_i$  with it's **output**
  2. Assign  $v_i$  to the first table  $t_j$  that can accept it
  3. Repeat from (1) until only one table is left

#### 9.3.1.1 Modified Bin Packing - Example

- Suppose *table size* is  $n = 3$  (ie. It's a *3LUT*)
  - Suppose *SOP expression* is  $f = ab + cd$
1. One table is created for  $ab$ , call it  $t_1$
  2.  $cd$  cannot fit in  $t_1$ , create another table  $t_2$  for it
  3. All terms finished. Let's pick  $t_1$  as the table with fewest number of unused variables
  4. Associate variable  $v_1$  with  $t_1$  (representing the table's output)
  5. Fit  $v_1$  into the unused **input** of  $t_2$
  6. Terminate algorithm, only one table ( $t_2$ ) left
  7. Final output of is  $f = v_1 + cd$ , which can be implemented by 2 *3LUTs*, compared to 3 *3LUTs* before

 


Figure 65: Modified Bin Packing

## 9.4 CLB packing

Usually, the CLB's in the FPGAs have more than a single LUT within them.

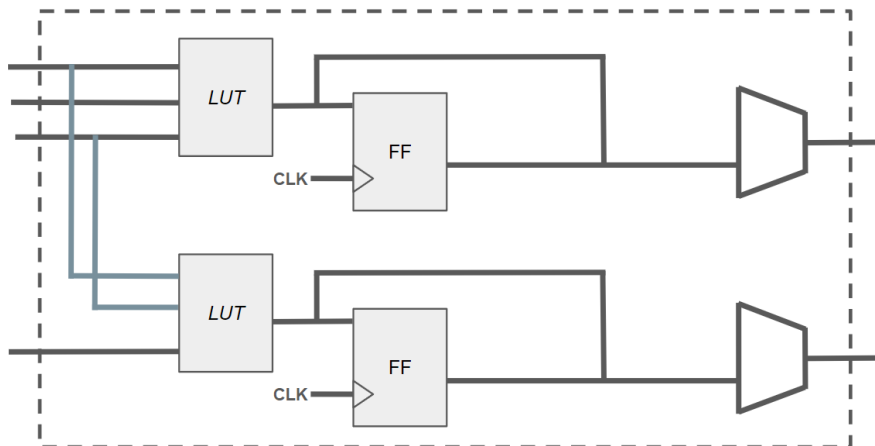


Figure 66: Logic Block  
Observe that the LUTs can share inputs as well

*Logic block packing* packs several LUTs and registers into one logic block under the following constraints

- Number of LUTs in a logic block
- Number of **distinct** input signals

Therefore, our optimization goal is to ...

- Pack LUTs st. routing signals are **minimized** between logic blocks
  - External routing is expensive, internal routing within the logic block is cheaper
- Fill each logic block to it's maximal capacity, to reduce to total number of logic blocks in the FPGA fabric

We can apply the same ideas of 'bin-packing' as covered in the previous sections.

## 9.5 Summary

Technology mapping on FPGAs involves ...

- Mapping
- Covering
- **Packing**